



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Amplifier and Comparator Circuits](#) > APP 529

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Automotive](#) > APP 529

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Power-Supply Circuits](#) > APP 529

Keywords: step-up controller, input converter, transformer flyback, flyback converter

APPLICATION NOTE 529

15V Input Converter Generates -185V at 50mA

Nov 01, 2000

Abstract: This design note shows how a 15V input flyback converter generates -185V at 50mA. The circuit uses the MAX668 step-up controller and a transformer to make a flyback converter.

Additional information:

- [Data sheet for the MAX668](#)
- [Data sheet for the MAX4130](#)
- [Technical support: power](#)

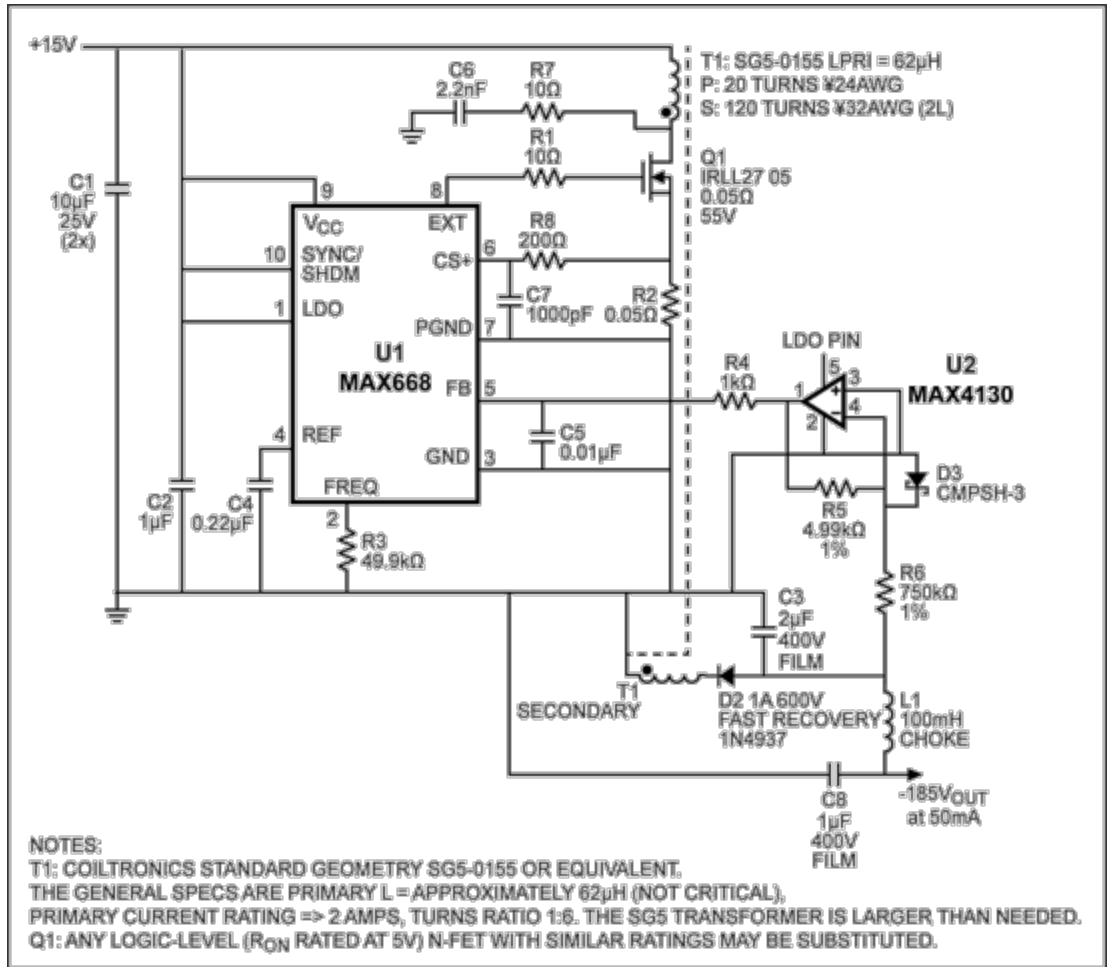


Figure 1. This circuit uses the MAX668 and a transformer (which will need about a one-to-six turns ratio) to make a flyback converter. The op amp inverts the feedback from the negative output voltage.

The circuit above generates -185V at 50mA from a +15V input. Based on a MAX668 transformer flyback application, the circuit employs a custom transformer to generate -185V through a combination of turns ratio and duty cycle. The transformer is designed on an SG5-size bobbin to facilitate the winding and to decrease the leakage inductance.

D2 is chosen as a fast-recovery diode to moderate the cost for a high-breakdown voltage part. Because the diode will see 185V + (6 × V_{IN}) + flyback due to leakage inductance, a 600V rating is necessary. C3 is chosen as a film capacitor to get high voltage rating and high ripple-current capacity. A secondary LC (L1 and C8) reduces output ripple from 100mV_{P-P} to less than 5mV_{P-P}.

Related Parts		
MAX4130	Single/Dual/Quad, Wide-Bandwidth, Low-Power, Single-Supply Rail-to-Rail I/O Op Amps	Free Samples
MAX668	1.8V to 28V Input, PWM Step-Up Controllers in μMAX	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 529: <http://www.maximintegrated.com/an529>

APPLICATION NOTE 529, AN529, AN 529, APP529, Appnote529, Appnote 529

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>